POLITECHNIKA ŚWIĘTOKRZYSKA		
loT laboratorium 3		
Kierunek: Informatyka	Rok: IV	Semestr: VII
Wykonał: Krzysztof Siwoń		

I

1. Wstęp

Głównym celem ćwiecznia było stworzenie symulacji schematu sterowanego przez moduł MCU.


MCU - MicroController Unit - scalony system mikroprocesorowy, zrealizowany w postaci pojedynczego układu scalonego zawierającego jednostkę centralną (CPU), pamięć RAM oraz rozbudowane układy wejścia-wyjścia i na ogół pamięć programu jako FRAM, MRAM, ROM lub Flash.

Schemat tworzony był w programie PacketTracer

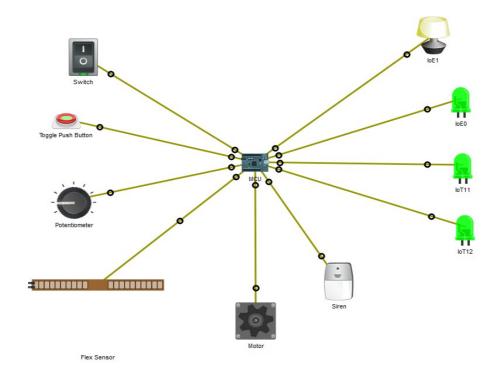2. Przebieg ćwiczenia:

- Do kontrolera MCU podłączyliśmy:
- Przełącznik, sterujący światłem
- Włącznik, kontrolujący LEDy
- > Potencjometr, ustawiający głośnośc Syreny
- > Flex Sensor, sterujący motor,
- ➤ Silnik (motor)
- > Syrena
- ➤ Diody LED
- ➤ Lampa (light)

W celu interakcji z danym elementem, należy nacisnąć na klawiaturze Alt+click.



Do połącznia elementów uzyliśmy IoT Custom Cable.

Następnie należało zaprogramować kontroler MCU aby cały układ spełniał założenia.

from gpio import * # imports all modules in the GPIO library from time import * # imports all modules in the time library

switchValue = 0 # initialize Switch sensor value global variable to $0 \mod P$ togglePushButtonValue = 0 # initialize Toggle Push Button sensor value global variable to $0 \mod P$ together value = 0 # initialize Potentiometer sensor value global variable to $0 \mod P$ flexSensorValue = 0 # initialize Flex Sensor value global variable to $0 \mod P$

def readFromSensors():

global switchValue # declare switchValue as global global togglePushButtonValue # declare togglePushButtonValue as global global potentiometerValue # declare potentiometerValue as global global flexSensorValue # declare flexSensorValue as global

switchValue = digitalRead(0) # read Switch sensor value togglePushButtonValue = digitalRead(1) # read Toggle Push Button sensor value potentiometerValue = analogRead(A0) # read Potentiometer sensor value flexSensorValue = analogRead(A1) # read Flex Sensor value

def writeToActuators():

```
otherwise false
              customWrite(2, "2") # turn on the Light
       else:
              customWrite(2, "0") # turn off the Light
       if (togglePushButtonValue == HIGH): # evaluates to True if the Toggle Push Button sensor
value is digital HIGH, otherwise false
              digitalWrite(3, HIGH)
       else:
              digitalWrite(3, LOW) # turn off the LED
       if (potentiometer Value > 512): # evaluates to True if the Potentiometer is turned at least half
way
              customWrite(4, HIGH) # turn on the Siren
       else:
              customWrite(4, LOW) # turn off the Siren
       if (flexSensorValue > 0): # evaluates to True if the Flex Sensor is bent, otherwise false
              analogWrite(5, flexSensorValue) # turn on the motor with speed equal to the Flex
Sensor value
       else:
              analogWrite(5, 0) # turn off the motor
       if(togglePushButtonValue ==HIGH):
              digitalWrite(9, HIGH)
       else:
              digitalWrite(9,LOW)
       if(togglePushButtonValue ==HIGH):
              digitalWrite(8, HIGH)
       else:
              digitalWrite(8,LOW)
def main(): # defines the main function
       pinMode(0, IN) # sets digital slot 0 (Switch) to input
       pinMode(1, IN) # sets digital slot 1 (Toggle Push Button) to input
       pinMode(2, OUT) # sets digital slot 2 (Light) to output
       pinMode(3, OUT) # sets digital slot 3 (LED) to output
       pinMode(4, OUT) # sets digital slot 4 (Siren) to output
       pinMode(5, OUT) # sets digital slot 5 (LED) to output
       while True: # loop indefinitely
              readFromSensors() # call the readFromSensors function
              writeToActuators() # call the writeToActuators function
              delay(1000) # delay script execution for 1000 ms
if name == " main ": # Evaluates to True if this module is the script being executed,
otherwise False if this module is being imported into another module
       main() # call the main function
```

if (switchValue == HIGH): # evaluates to True if the Switch sensor value is digital HIGH,

Założenie zadania przewidywało sterowanie 8diodami LED. Udało mi się wykonać w/w zadanie tylko dla 3 diód.

3. Wnioski

Dzięki programowi PacketTracer poznaliśmy zasady działania poszczególnych kontrolerów, napisaliśmy skrypt, który sterował poszczególnymi modułami. Pokazało to, jaki potencjał istnieje w IoT, jak sami możemy zbudować i kontrolować elementy obsługujące np. SmartDom.